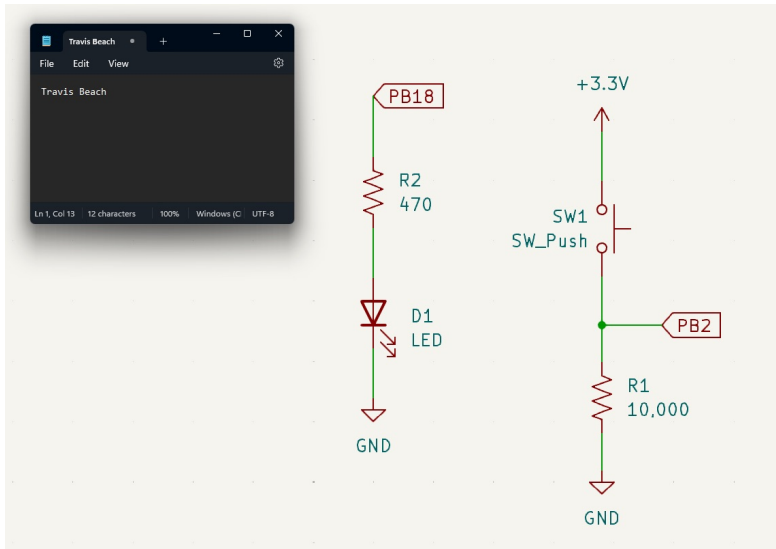


Circuit Diagram:



Estimated LED:

$$3.2V = 470\Omega I_R + \frac{I_d + 32}{20}$$

$$I_d = 20V_d - 32$$

$$I \text{ in mA} \quad 3.2 = 0.470 I + \frac{I + 32}{20}$$

$$V_d = \frac{I_d + 32}{20} = 1.755V$$

$$64 = 9.4I + I + 32$$

$$I_d = 3.1mA \quad V_d = 1.76V$$

$$32 = 10.4I$$

$$I = 3.1mA$$

Switch Measurements:

Input V	0V	} not pressed
Resistor I	0mA	
Input V	3.264V	} pressed
Resistor I	0.3346mA	

LED Measurements:

LED V 0V LED off

LED I 0V LED off


LED V 1.849V LED on

LED I 2.856mA LED on

LED P 5.281mW LED on

Period / Frequency: Period = 20ms, Frequency = 49.4

Terminal:

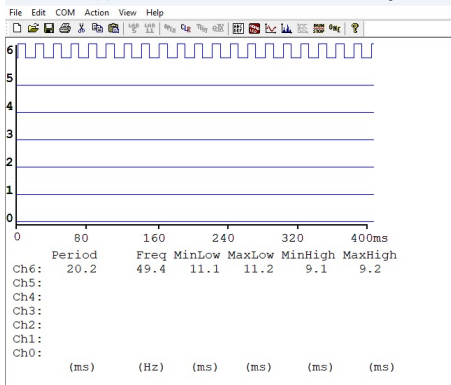

ECE319K Lab 2, Spring 2025  
Student EID= TMB3956  
Running the grader  
15,34,75,45, Perfect, Score=25  
End of Lab 2, Spring 2025

Duty Cycle Switching:

